



**Figure 1** This basic circuit combines a current-output DAC, IC<sub>1</sub>, with a single-ended-to-differential op-amp stage—IC<sub>2</sub>, IC<sub>3A</sub>, and IC<sub>3B</sub>—to generate the desired outputs.